

# RF and Microwave Transmission Lines


ELEC 2230

## *Section 5*

Roger D. Pollard  
School of Electronic & Electrical Engineering  
The University of Leeds


February 2004

### The network analyzer

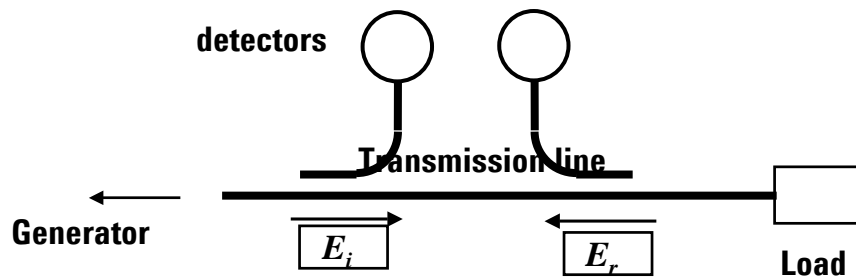

$$\Gamma = \frac{E_r}{E_i}$$

## The network analyzer

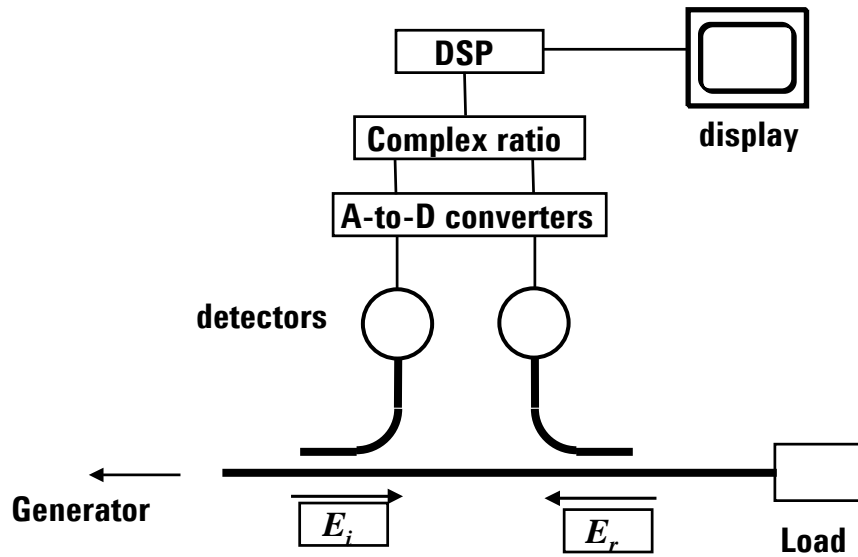


ELEC 2230  
Feb 2004

Page 3

## The network analyzer

### Transmission measurement

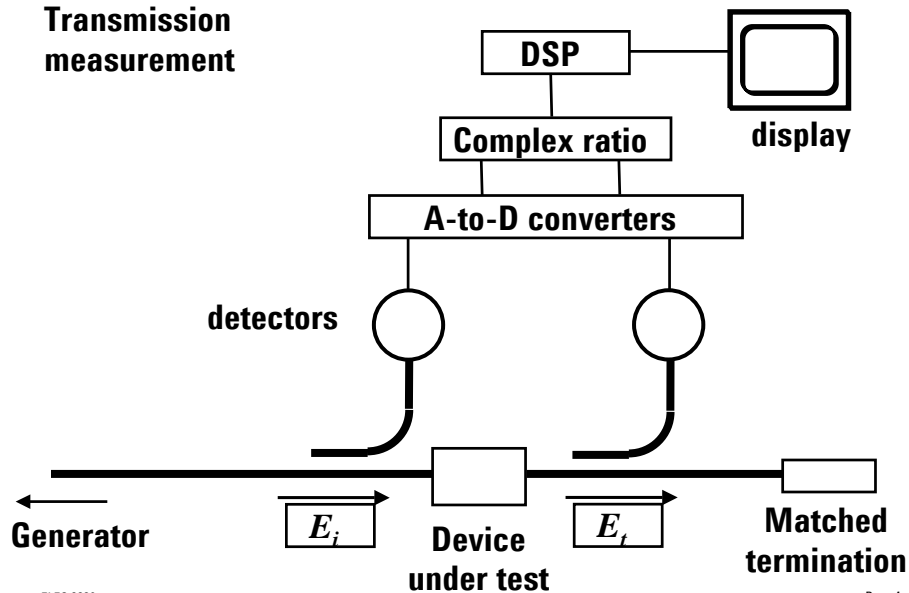


ELEC 2230  
Feb 2004

Page 4

## Impedance and Admittance relationships

Termination impedance is, in general, complex

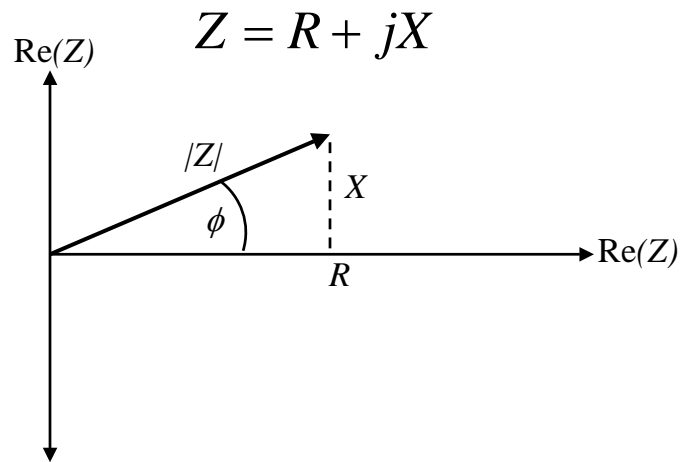


ELEC 2230  
Feb 2004

Page 5

## Reactance chart


Normalised to  $Z_0$

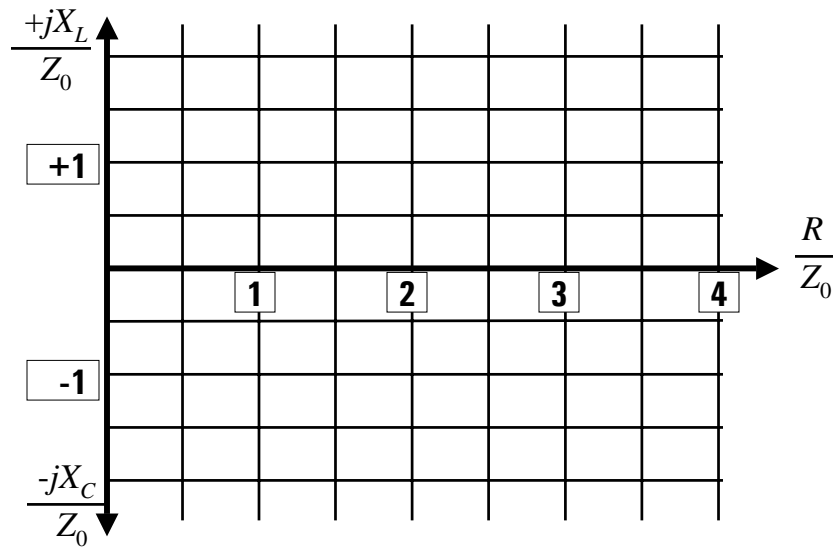

ELEC 2230  
Feb 2004

Page 6

## Terminated lossless transmission line

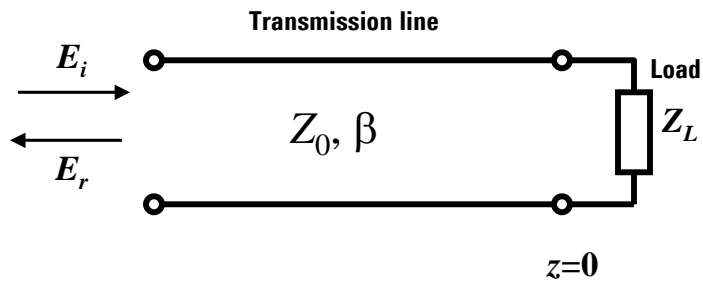

## Terminated lossless transmission line

Incident wave  $E_i = V^+ e^{-j\beta z}$

Reflected wave  $E_r = V^- e^{+j\beta z}$

Ratio of voltage to current for travelling wave on the transmission line must be  $Z_0$

But since the termination  $Z_L \neq Z_0$  the ratio of voltage to current at the load must be  $Z_L$  and a reflected wave must be excited to satisfy that condition.

## Terminated lossless transmission line

**Total voltage**

$$V(z) = E_i + E_r = V^+ e^{-j\beta z} + V^- e^{+j\beta z}$$

**Total current**

$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z}$$

**So, at the load, where  $z = 0$**

## Terminated lossless transmission line

**So, at the load, where  $z = 0$**

$$Z_L = \frac{V(0)}{I(0)} = \frac{V^+ + V^-}{V^+ - V^-} Z_0$$

**Now, solve for**

$$V^- = \frac{Z_L - Z_0}{Z_L + Z_0} V^+$$

## Terminated lossless transmission line

Recall that the reflection coefficient is

$$\Gamma = \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

And can write the total voltage and current as

$$V(z) = V^+ \left[ e^{-j\beta z} + \Gamma e^{+j\beta z} \right]$$

$$I(z) = \frac{V^+}{Z_0} \left[ e^{-j\beta z} - \Gamma e^{+j\beta z} \right]$$

## Terminated lossless transmission line

At any point on the line, (  $z = -l$  )

$$\Gamma(l) = \frac{V^- e^{-j\beta l}}{V^+ e^{+j\beta l}} = \Gamma(0) e^{-2j\beta l}$$

**So note that, as you move along the line, the magnitude of the reflection coefficient is unchanged. The phase of the reflection coefficient increases by  $2\beta l$  - the electrical length.**

## Terminated lossless transmission line

Or the impedance seen looking in to the line  
looking towards the load is

$$\begin{aligned} Z_{in} &= \frac{V(-l)}{I(-l)} = \frac{V^+ \left[ e^{+j\beta l} + \Gamma e^{-j\beta l} \right]}{V^+ \left[ e^{+j\beta l} - \Gamma e^{-j\beta l} \right]} Z_0 \\ &= \frac{\left[ 1 + \Gamma e^{-2j\beta l} \right]}{\left[ 1 - \Gamma e^{-2j\beta l} \right]} Z_0 \end{aligned}$$

## Transmission line impedance equation

Can re-arrange as

$$\begin{aligned} Z_{in} &= Z_0 \frac{(Z_L + Z_0)e^{+j\beta l} + (Z_L - Z_0)e^{-j\beta l}}{(Z_L + Z_0)e^{+j\beta l} - (Z_L - Z_0)e^{-j\beta l}} \\ &= Z_0 \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} \\ &= Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \end{aligned}$$

## The Smith Chart

Tool to help understand and solve transmission line problems


It is a polar plot of reflection coefficient  $\Gamma$  overlaid with contours of constant resistance and reactance

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1} = \frac{z - 1}{z + 1}$$

ELEC 2230  
Feb 2004

Page 15

## The Smith Chart

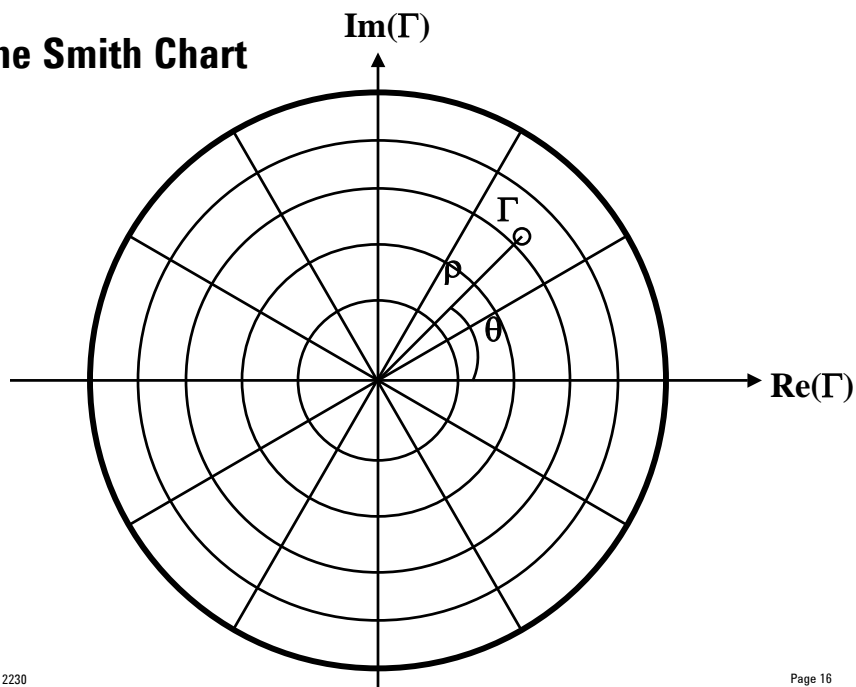

ELEC 2230  
Feb 2004

Page 16



## The Smith Chart

Now consider some specific values of  $Z_L$

(a) Short circuit:  $Z_L = 0$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} = -1$$

## The Smith Chart

Now consider some specific values of  $Z_L$

(b) Open circuit:  $Z_L = \infty$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1 - \frac{Z_0}{Z_L}}{1 + \frac{Z_0}{Z_L}} = \frac{1 - \frac{Z_0}{\infty}}{1 + \frac{Z_0}{\infty}} = +1$$

## The Smith Chart

Now consider some specific values of  $Z_L$

**(c) Match:**  $Z_L = Z_0$  ( $z = 1$ )

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z - 1}{z + 1} = 0$$

## The Smith Chart

Now consider some specific values of  $Z_L$

**(d) Inductor:**  $z = 0 + j1$

$$\Gamma = \frac{z - 1}{z + 1} = \frac{j - 1}{j + 1} = \frac{(j - 1)(-j + 1)}{(j + 1)(-j + 1)} = j$$

**(e) Capacitor:**  $z = 0 - j1$

$$\Gamma = \frac{z - 1}{z + 1} = \frac{-j - 1}{-j + 1} = \frac{(-j - 1)(j + 1)}{(-j + 1)(j + 1)} = -j$$

## The Smith Chart

Now consider some specific values of  $Z_L$

(d) Inductive impedance:  $z = 1 + j1$

$$\Gamma = \frac{z-1}{z+1} = \frac{1+j-1}{1+j+1} = \frac{j}{2+j} = \frac{1+2j}{5}$$


(e) Capacitive impedance:  $z = 1 - j1$

$$\Gamma = \frac{z-1}{z+1} = \frac{1-j-1}{1-j+1} = \frac{-j}{2-j} = \frac{1-2j}{5}$$

ELEC 2230  
Feb 2004



Page 21

## The Smith Chart

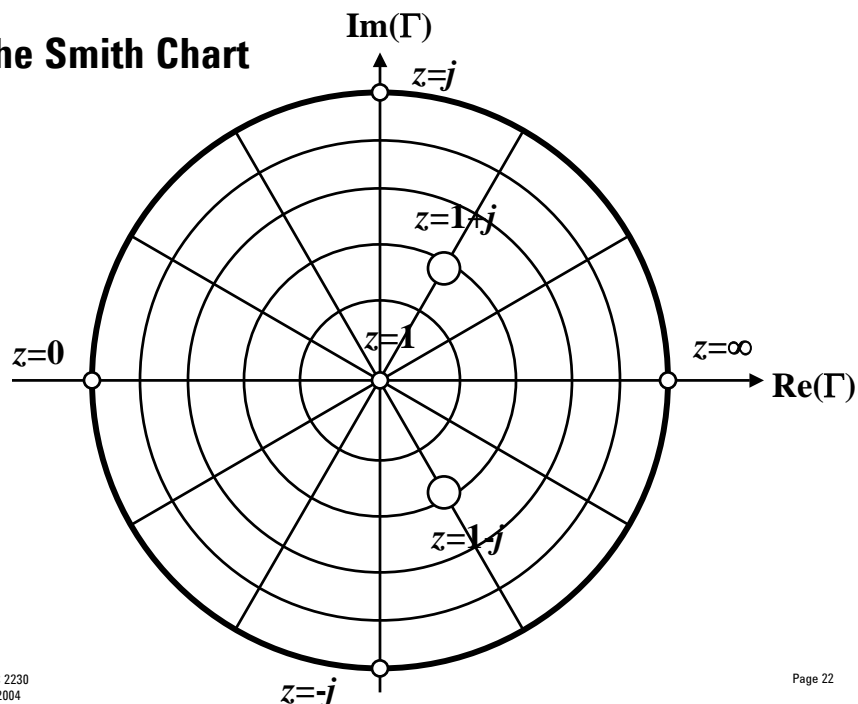


ELEC 2230  
Feb 2004

Page 22

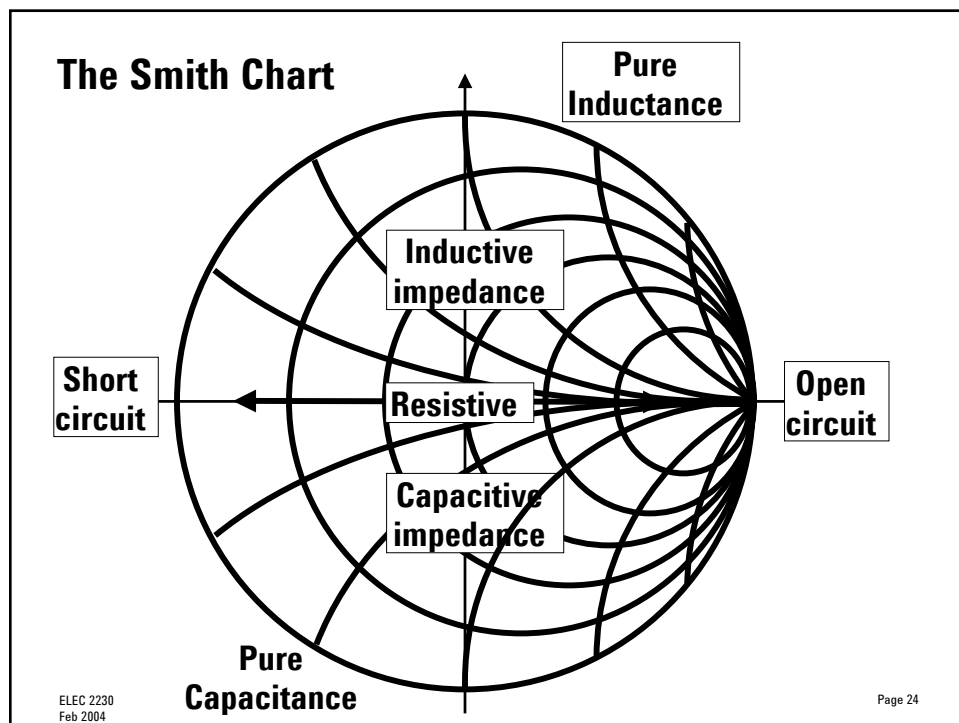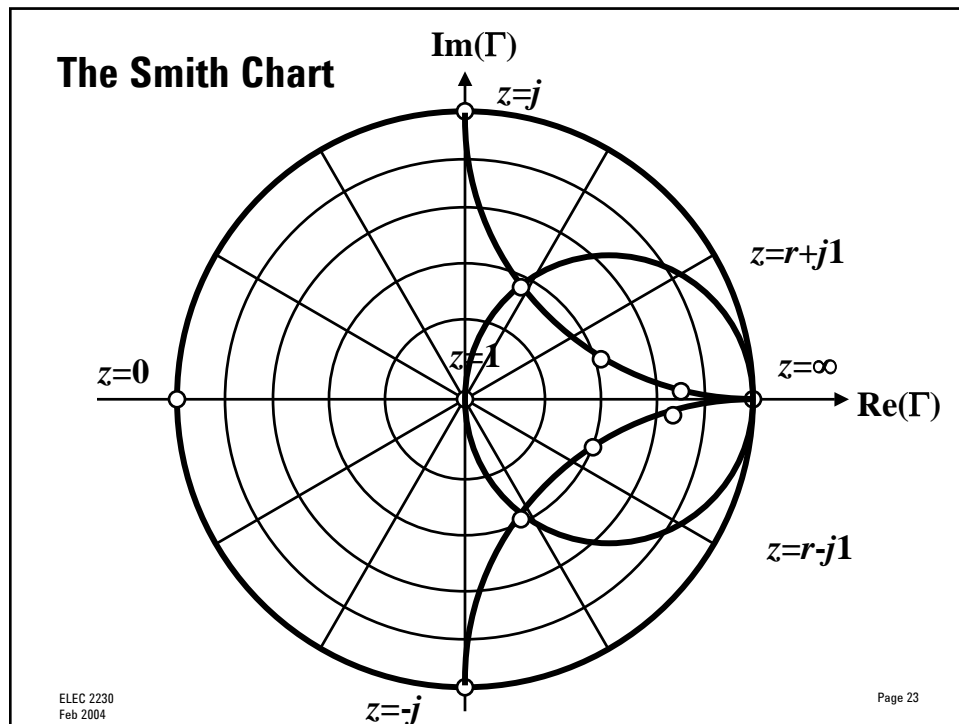


## The Smith Chart

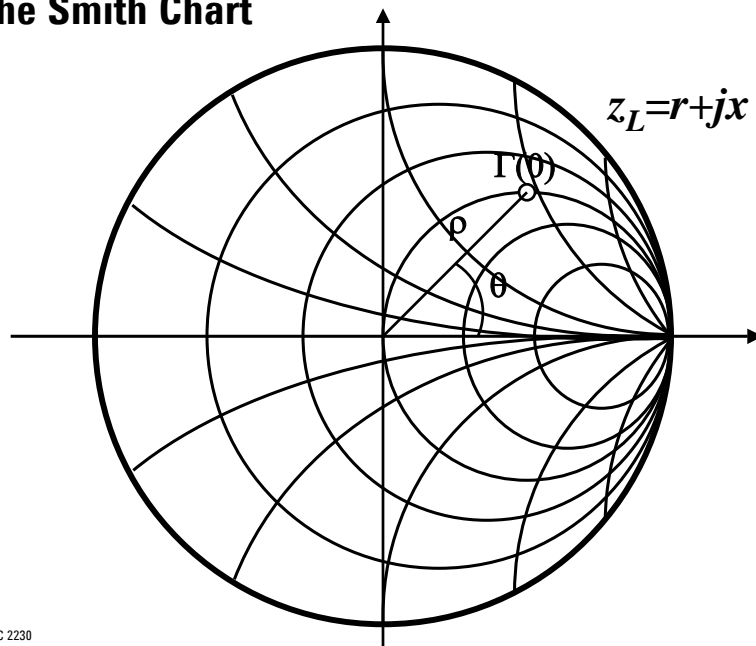

ELEC 2230  
Feb 2004

Page 25


## The Smith Chart

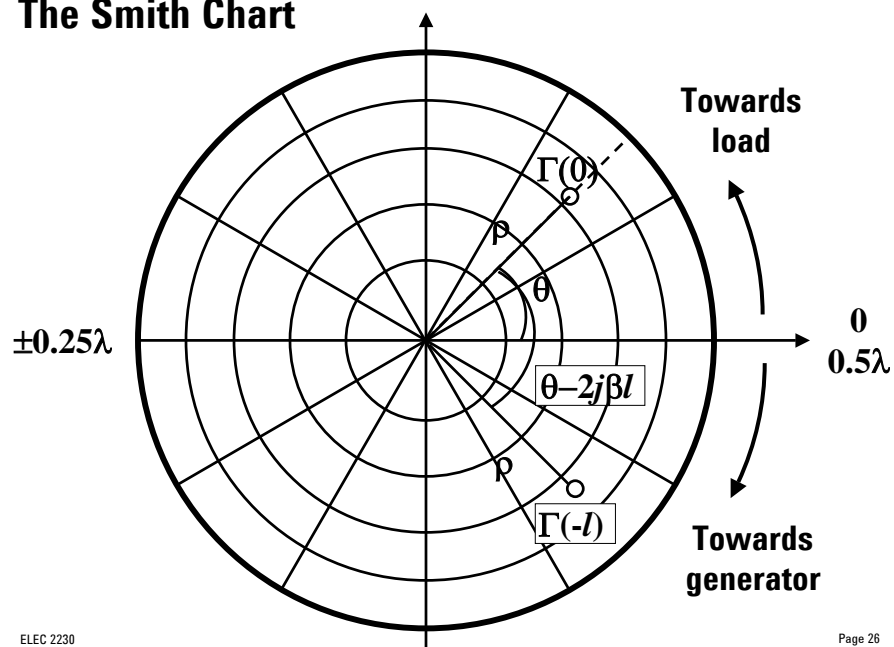

ELEC 2230  
Feb 2004

Page 26

## The Smith Chart

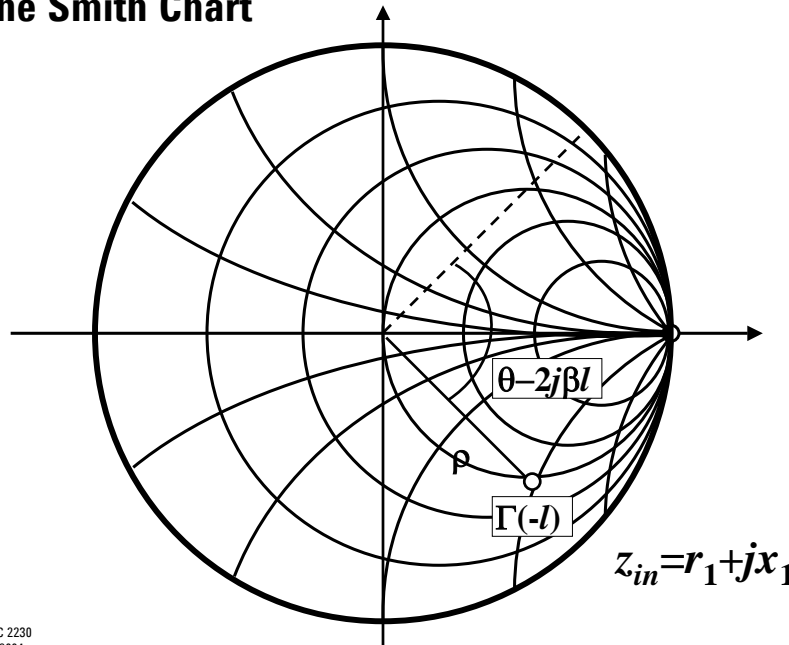

ELEC 2230  
Feb 2004

Page 27